



Faculty of Engineering and Technology Department  
of Electrical and Computer Engineering

ENCS 2110

**Digital Electronics and Computer Organization**  
**Lab Experiment No. 4- Digital Circuits**  
**Implementation using Breadboard (POST Lab)**

<b>Name:</b>	<b>Zainab murad ismail</b>
<b>ID:</b>	<b>1211020</b>
<b>Instructor:</b>	<b>Ashraf Al-Rimawi</b>
<b>Section:</b>	<b>4</b>


**1. How do you go about adding an Enable (E) signal to the decoder in Figure 4.7? Modify the implementation to show that. (Design Only using chips in Figure 1).**

We can do this By adding a third Input to the AND gates which will be the Enable.


If the Enable =0 all the outputs will be zero no matter the inputssince all the AND Gates won't work.

If the Enable equals One it will work like a normal Decoder Since the Enable won't affect anything.

When using the IC there is no 3 input AND gate so what we Do is use two AND gates instead of a Three input AND Gate.

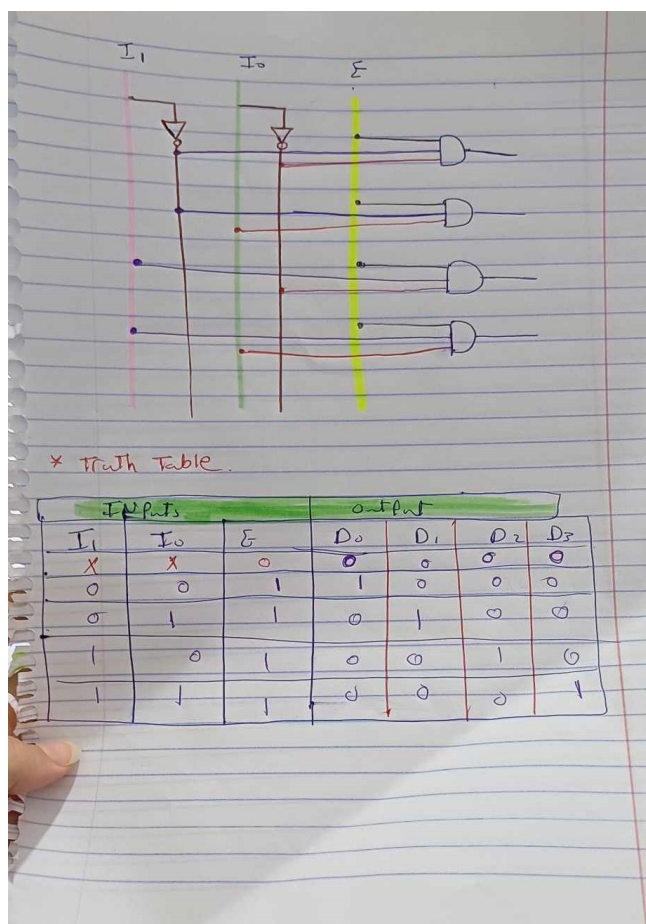


IO4

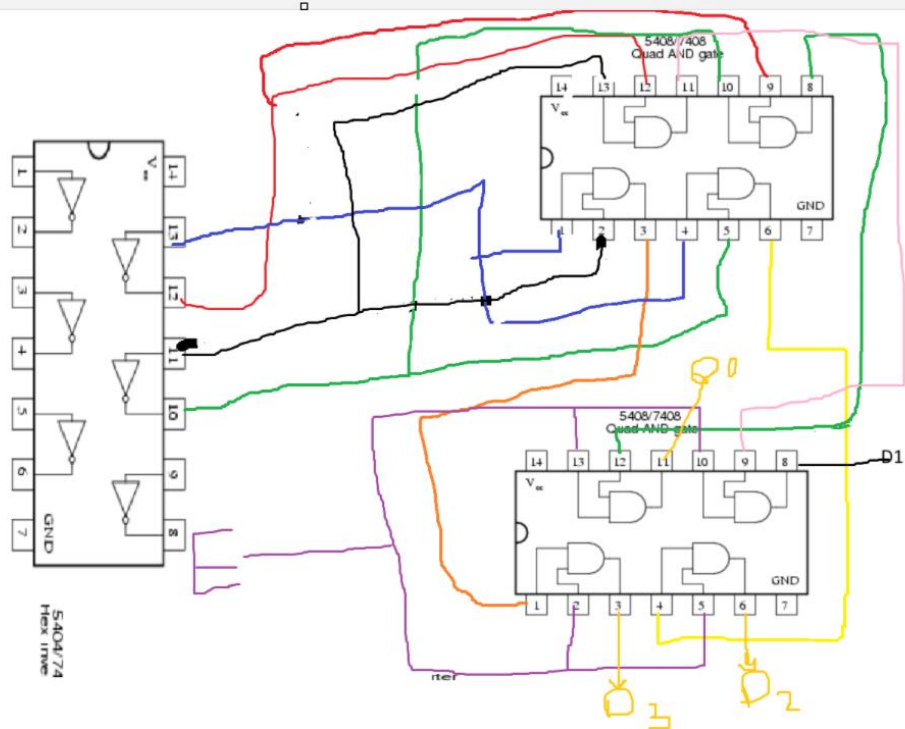

Act

 
## 2. How to use that to implement a 3x8 decoder using chips in Figure 1.

We make  $I_2$  the enable of both decoders, and use  $I_1$  and  $I_0$  as the inputs of the decoders.



3. Use the just constructed 4x1 multiplexer to design a three-input network that gives 1 if the majority of its inputs are 1 and outputs a zero otherwise (Design Only using chips in Figure 1).

A	B	C	OUTPUT	Output Equivalent : to
0	0	0	0	0
0	0	1	0	0
0	1	0	0	C
0	1	1	1	C
1	0	0	0	C
1	0	1	1	C
1	1	0	1	1
1	1	1	1	1

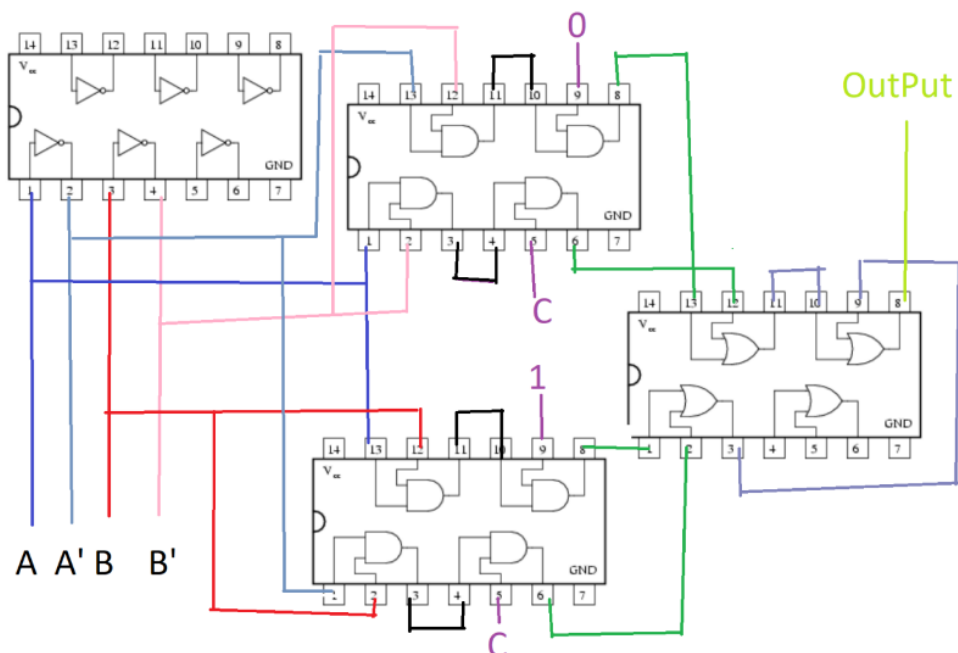

4. Implement  $f(x, y, z) = m(0, 1, 4, 6, 7)$ , using 4x1 MUX using chips in Figure 1.

X	Y	Z	F	Output Equivalent : to
0	0	0	1	1
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	'Z
1	0	1	0	'Z
1	1	0	1	1
1	1	1	1	1

